

# DLD ASSESSMENT 3

---

**NAME: ANSHIL SETH**

**REG. NUMBER: 18BCI0173**


**SLOT: L25 + L26**

**FACULTY: PROF. LIJO VP**

## QUESTION 1

- a. **AIM:** Design a combinational circuit with three inputs x,y and z and three outputs A,B and C using full adders and an inverter. When the binary input is 0,1,2 or 3 the binary output is one greater than the input. When the binary input is 4,5,6 or 7 the binary output is one less than the input.

### CIRCUIT DIAGRAM:

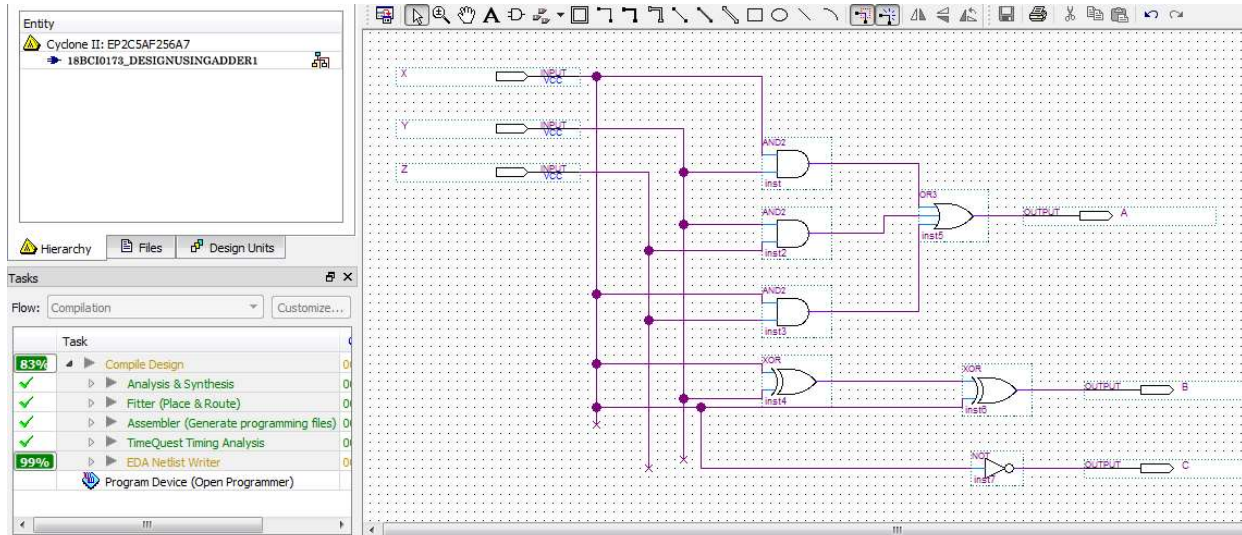

### TRUTH TABLE:


X	Y	Z	A	B	C
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0

### EXPRESSIONS:

$$A = YZ + XZ + XY$$


$$B = X \text{ xor } Y \text{ xor } Z$$

$$C = Z'$$

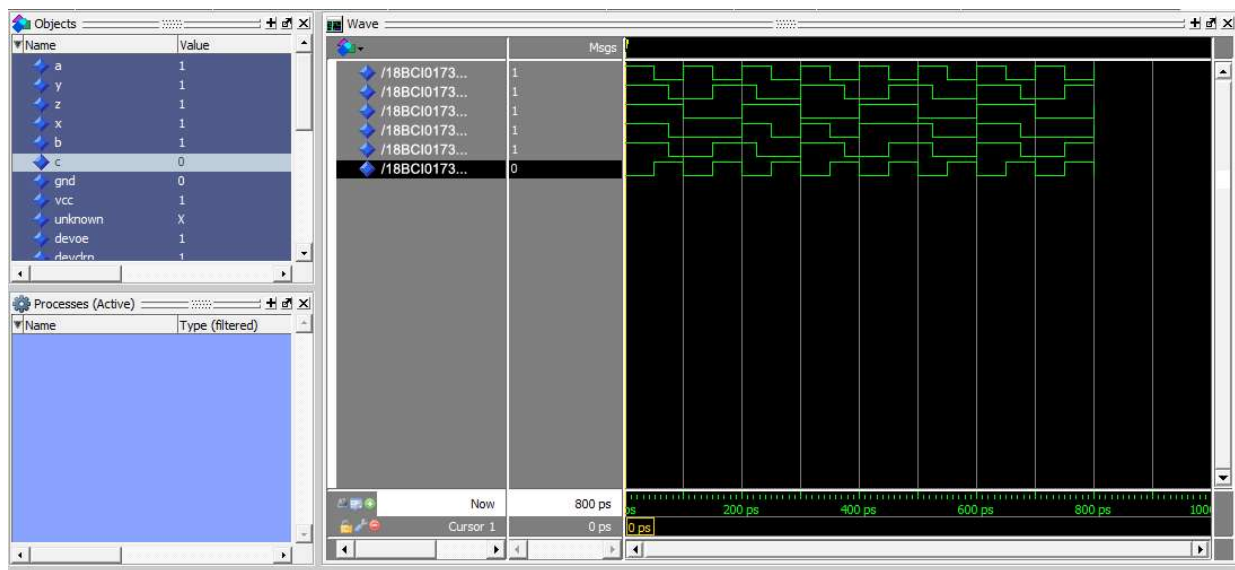**FINAL RESULT:**

**AIM:** implement the four Boolean functions listed using three half adders.

**CIRCUIT DIAGRAM:**

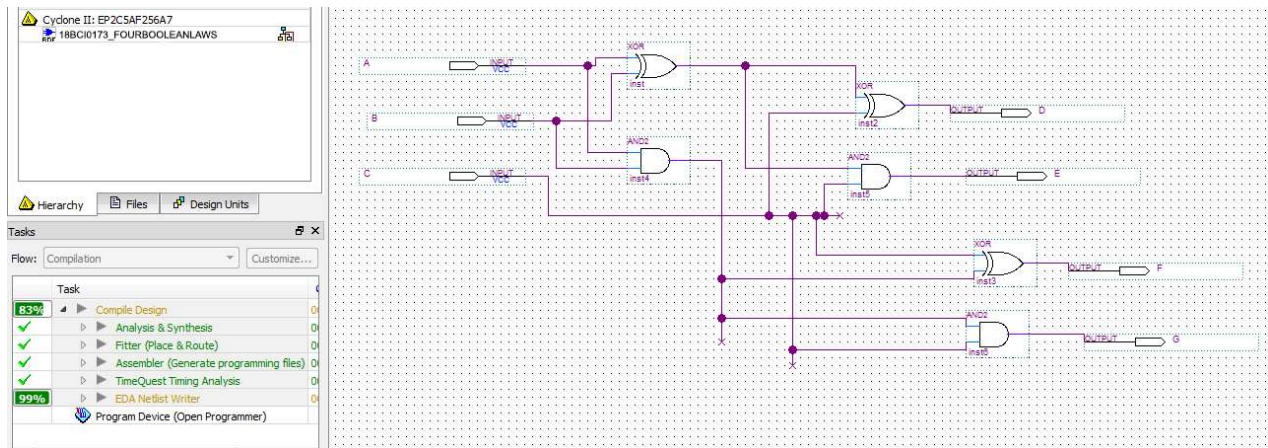

**TRUTH TABLE:**

A	B	C	D	E	F	G
0	0	0	0	0	0	0
0	0	1	1	0	0	0
0	1	0	1	0	0	0
0	1	1	0	1	1	0
1	0	0	1	0	1	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	1	0	1	1


**EXPRESSIONS:**

$$D = A \oplus B \oplus C$$

$$E = A'BC + AB'C$$


$$F = ABC' + (A' + B)C$$

$$G = G = ABC$$

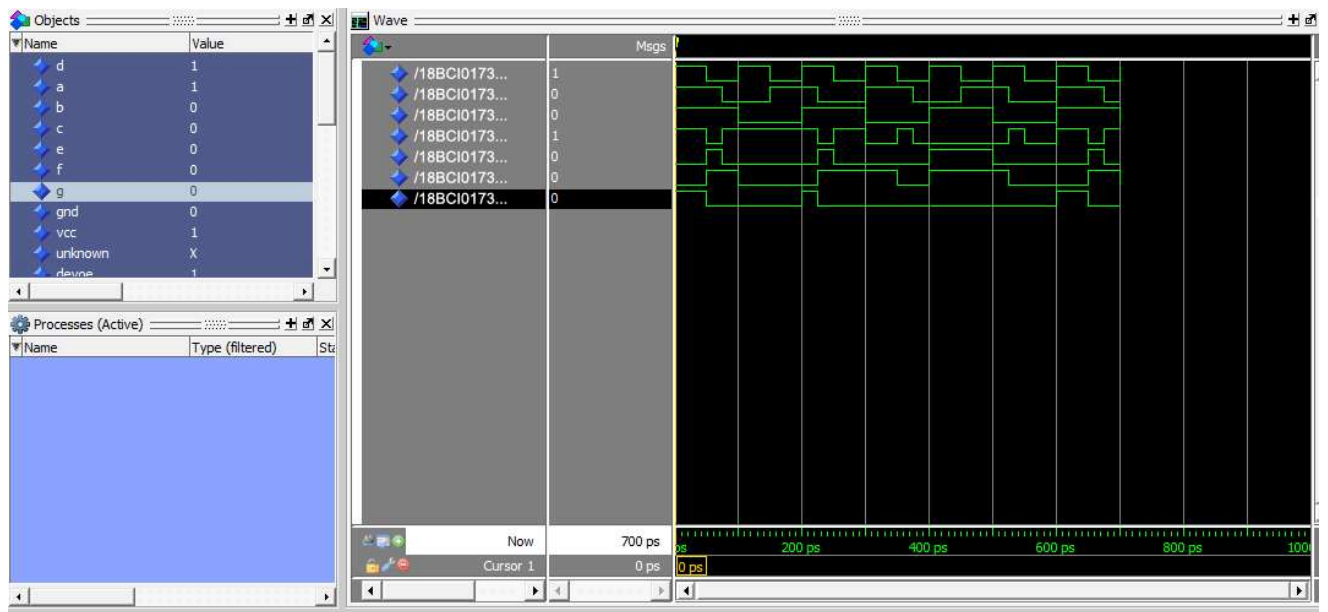**FINAL RESULT:**

c. **AIM:** design 2-bit parallel adder/subtractor circuit.


### CIRCUIT DIAGRAM:

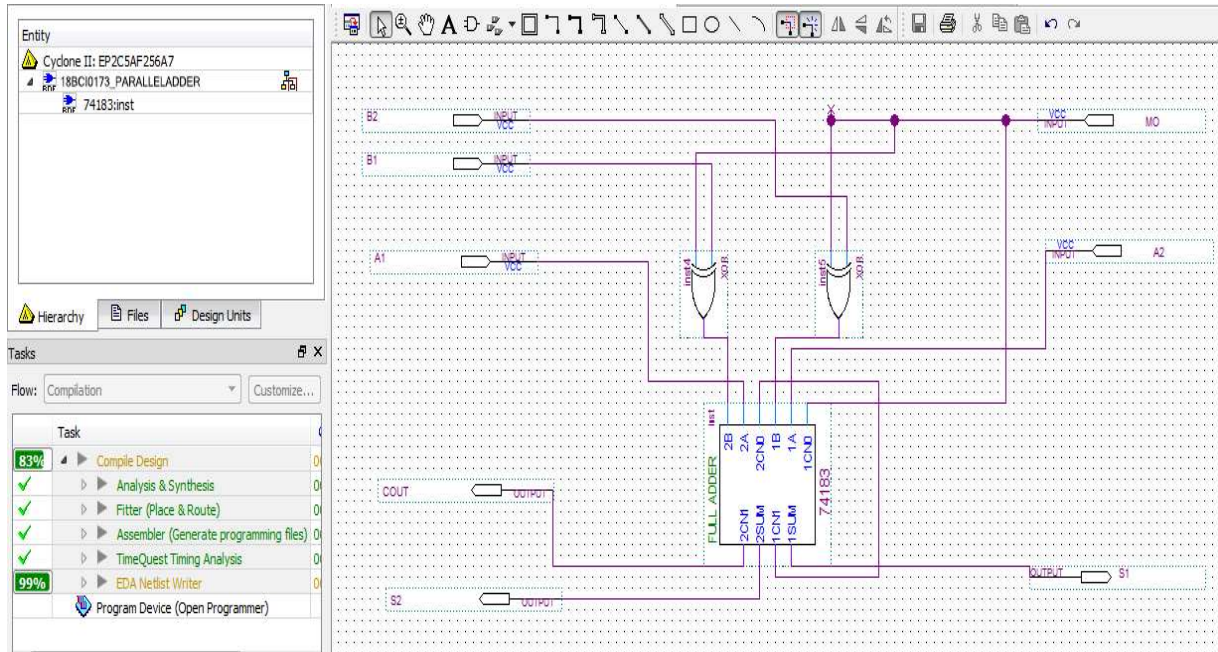

m=0 for addition of numbers a1 a2 and b1 b2

### TRUTH TABLE:

A2	A1	B2	B1	C	S1	S2
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

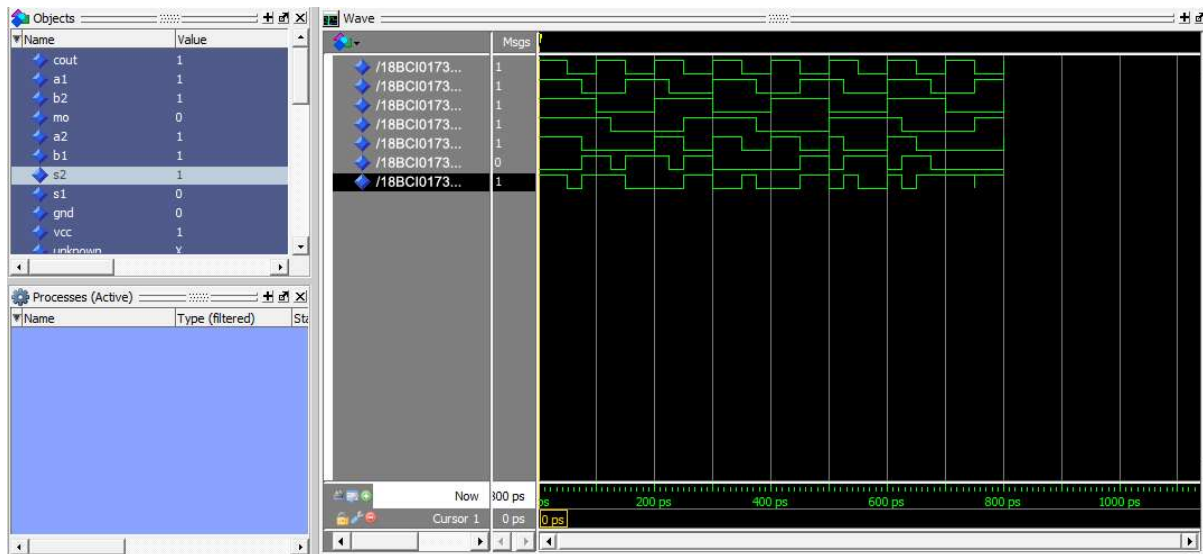
**ADDER FINAL RESULT:**

M=1 for subtraction of numbers a1 a2 and b1 b2.


A2	A1	B2	B1	C	S1	S2
0	0	0	0	0	0	0
0	0	0	1	1	1	0
0	0	1	0	1	0	1
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	0	0
0	1	1	0	1	1	0
0	1	1	1	1	0	1
1	0	0	0	0	1	0
1	0	0	1	0	0	1
1	0	1	0	0	0	0
1	0	1	1	1	1	0
1	1	0	0	0	1	1
1	1	0	1	0	1	0
1	1	1	0	0	0	1
1	1	1	1	0	0	0



### SUBTRACTOR FINAL RESULT:

 

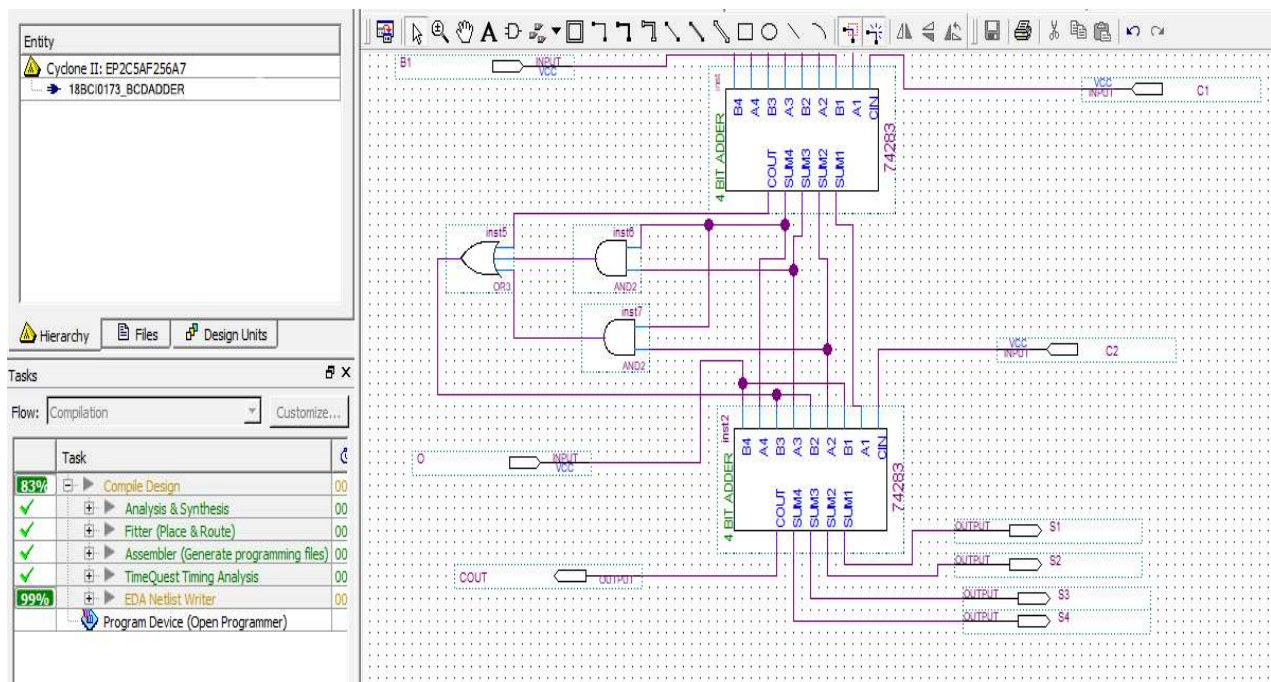
**AIM:** design a BCD adder using binary parallel adder.






**TRUTH TABLE:**

k	8	4	2	1	c	S4	S3	S2	S1	decimal
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19

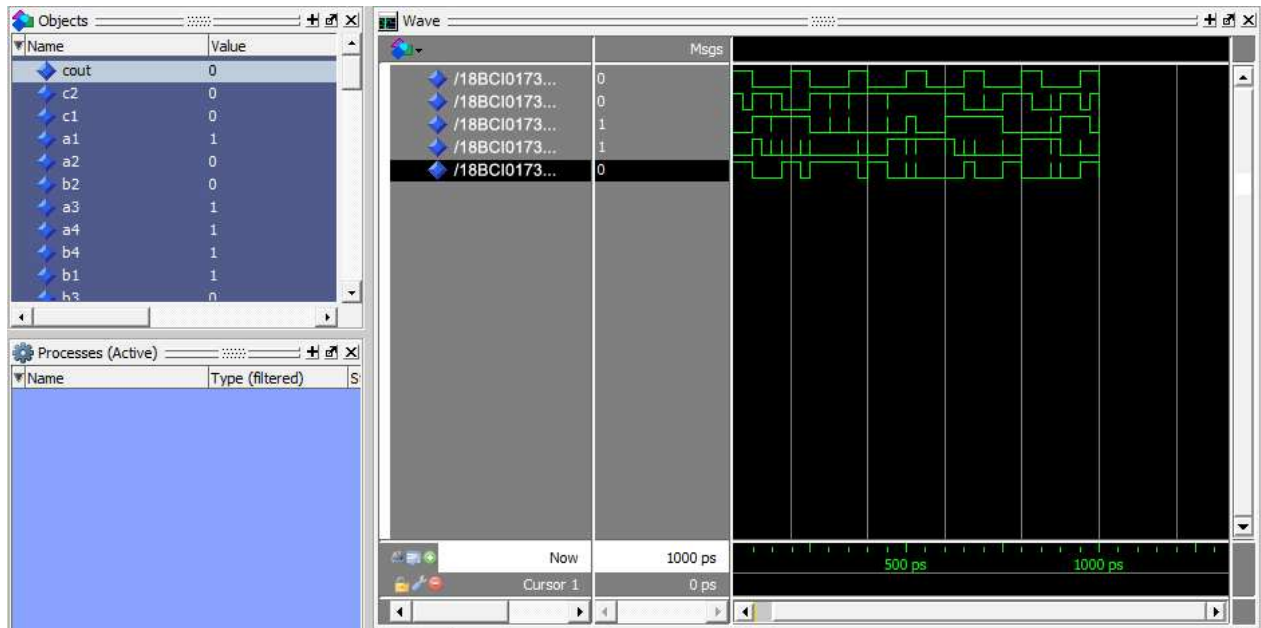**FINAL RESULT:**
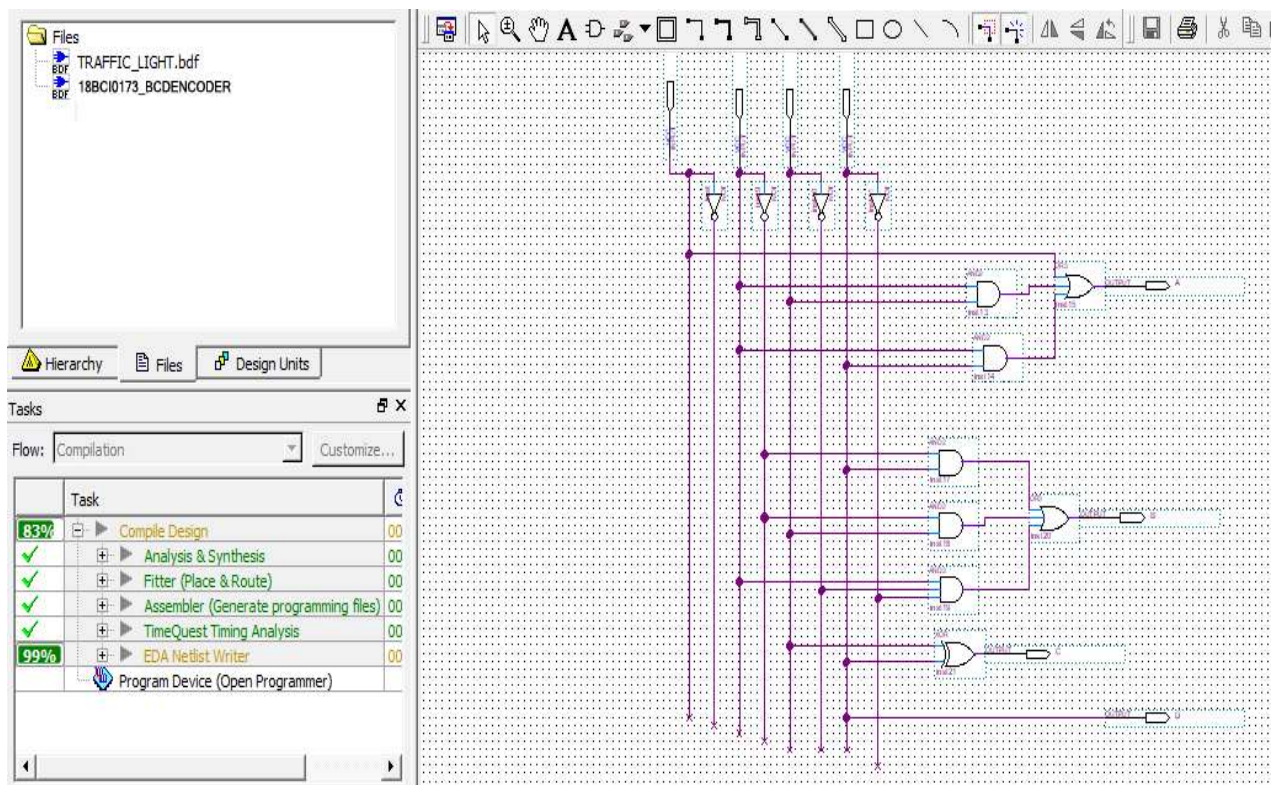
## QUESTION 2

**AIM:** design a circuit to convert 2421 to 84-2-1.



### TRUTH TABLE:

W	X	Y	Z	A	B	C	D	Decimal digit
0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	1	1	1
0	0	1	0	0	1	1	0	2
0	0	1	1	0	1	0	1	3
0	1	0	0	0	1	0	0	4
1	0	1	1	1	0	1	1	5
1	1	0	0	1	0	1	0	6
1	1	0	1	1	0	0	1	7
1	1	1	0	1	0	0	0	8
1	1	1	1	1	1	1	1	9


### EXPRESSIONS:

$$A = WX'YZ + WXY'Z' + WXY'Z + WXYZ' + WXYZ$$


$$B = W'X'Y'Z + W'X'YZ' + W'X'YZ + W'XY'Z' + WXYZ$$

$$C = W'X'Y'Z + W'X'YZ' + WX'YZ + WXY'Z' + WXYZ$$

$$D = W'X'Y'Z + W'X'YZ + WX'YZ + WXY'Z + WXYZ$$

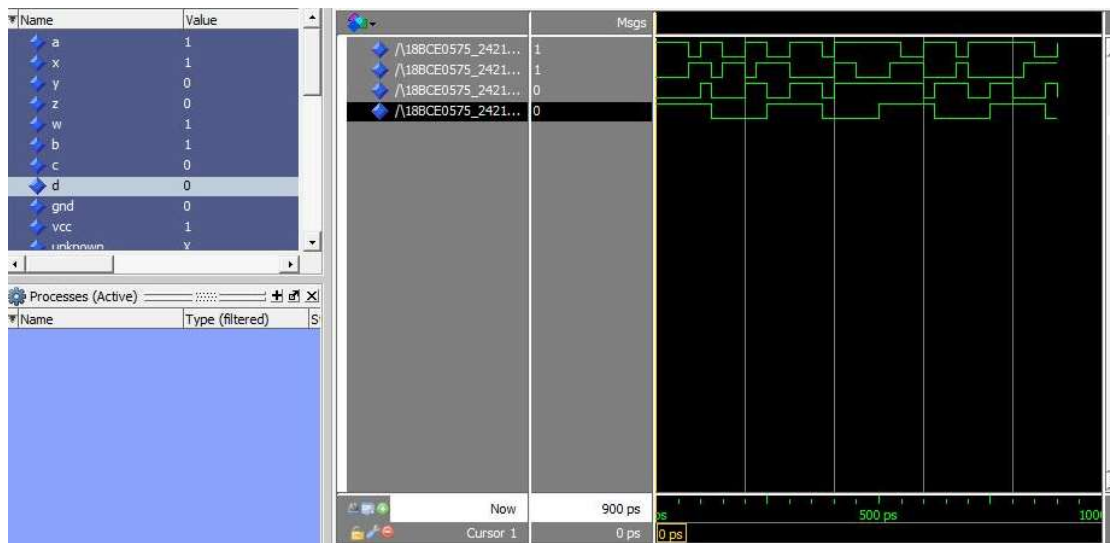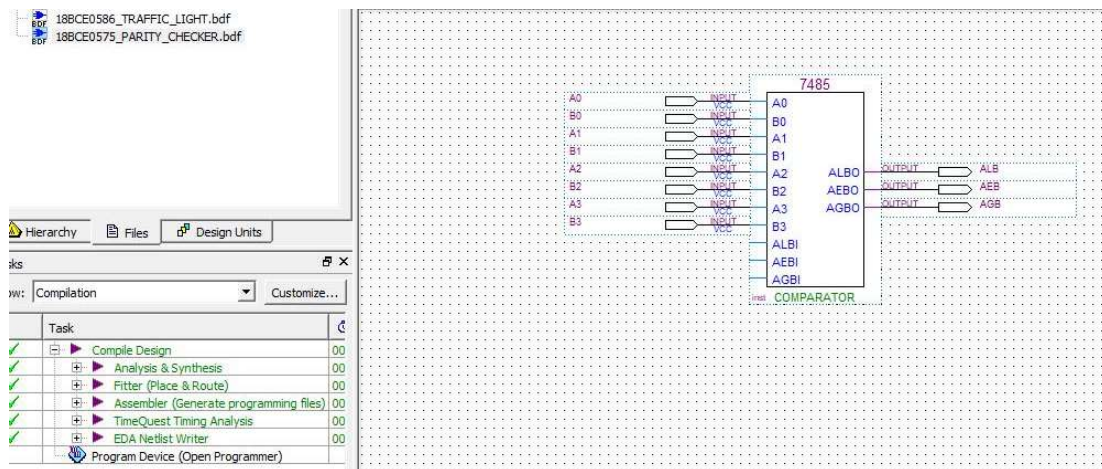**FINAL RESULT:**

**AIM:** Design a circuit to compare two 4 bit numbers using IC 7485.



#### TRUTH TABLE:


A	B	A<B	A=B	A>B
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

#### EXPRESSION:

**A EQUAL TO B:**  $(A0 \text{ XNOR } B0)(A1 \text{ XNOR } B1)(A2 \text{ XNOR } B2)(A3 \text{ XNOR } B3)$ .


**A GREATER THAN B:**  $A3B3' + (A3 \text{ XNOR } B3)A2B2' + (A3 \text{ XNOR } B3)(A2 \text{ XNOR } B2)A1B1' + (A3 \text{ XNOR } B3)(A2 \text{ XNOR } B2)(A1 \text{ XNOR } B1)A0B0'$

**A LESS THAN B:**  $A3'B3 + (A3 \text{ XNOR } B3)A2'B2 + (A3 \text{ XNOR } B3)(A2 \text{ XNOR } B2)A1'B1 + (A3 \text{ XNOR } B3)(A2 \text{ XNOR } B2)(A1 \text{ XNOR } B1)A0'B0$

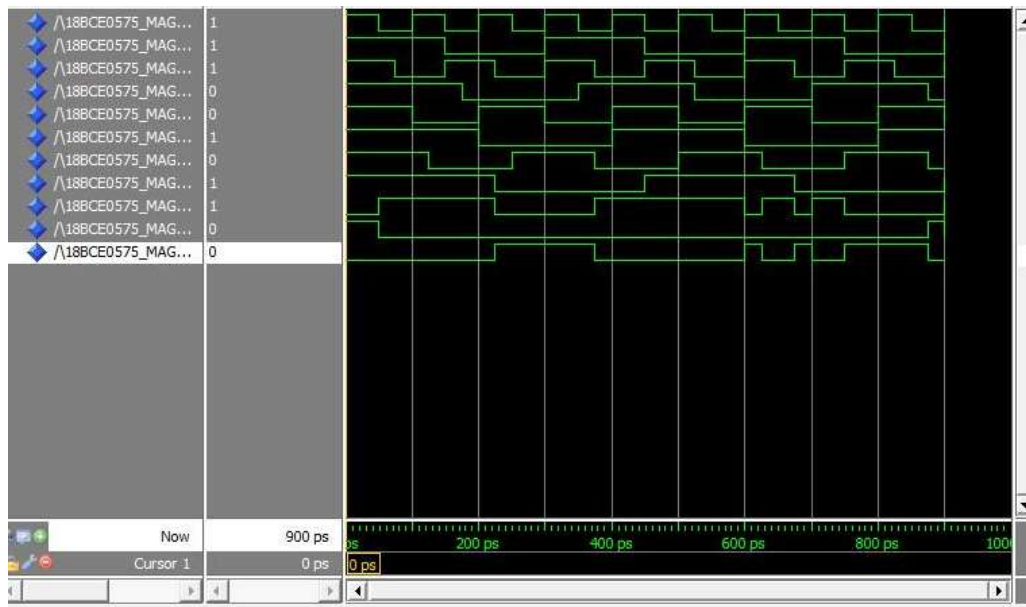**FINAL RESULT:**

**AIM:** To design BCD to seven segment display

**CIRCUIT DIAGRAM:**

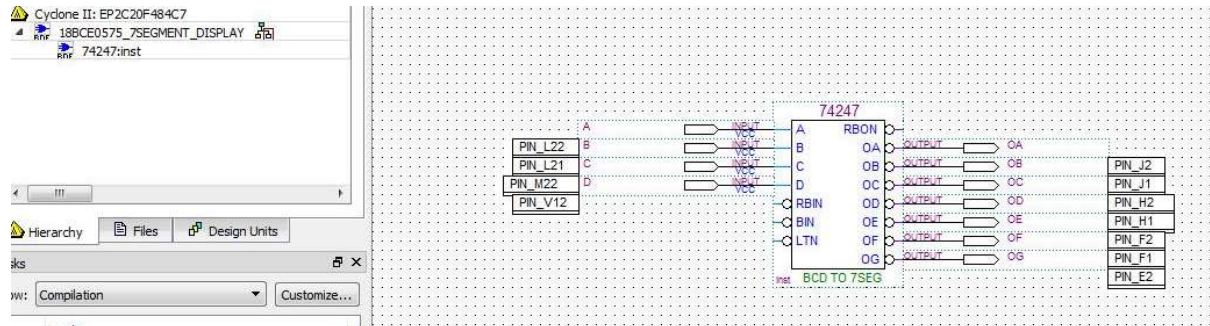


**TRUTH TABLE:**

A	B	C	D	OA	OB	OC	OD	OE	OF	OG
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1


**FINAL RESULT:**



 

**AIM:** Design a circuit to display thrice of a number on seven segment display (consider maximum input number to be 2 bit)

**CIRCUIT DIAGRAM:**

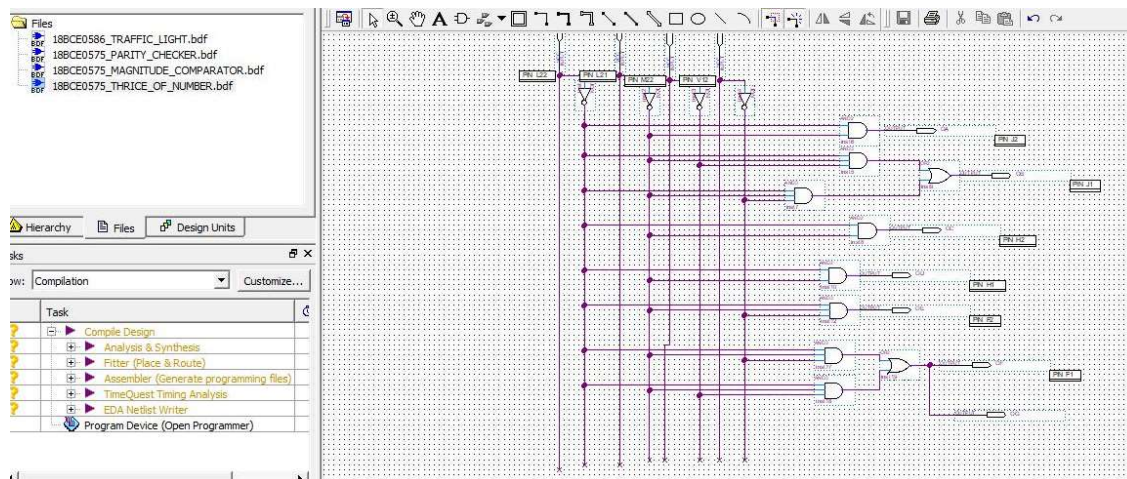

**TRUTH TABLE:**

A	B	C	D	OA	OB	OC	OD	OE	OF	OG
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	1	1	1	1	0	0	1
0	0	1	0	1	0	1	1	1	1	1
0	0	1	1	1	1	1	1	0	1	1

**EXPRESSIONS:**

$$OA = A'B'$$

$$OB = A'B'C' + A'B'D$$

$$OC = A'B'$$

$$OD = A'B'$$


$$OE = A'B'D'$$

$$OF = A'B'D' + A'B'C$$

$$OG = A'B'D + A'B'C$$


FINAL RESULT:

Thrice of 1

 




Thrice of 3

 

### QUESTION 3

- a. **AIM:** To design a 2 to 4 line decoder.

#### CIRCUIT DIAGRAM:

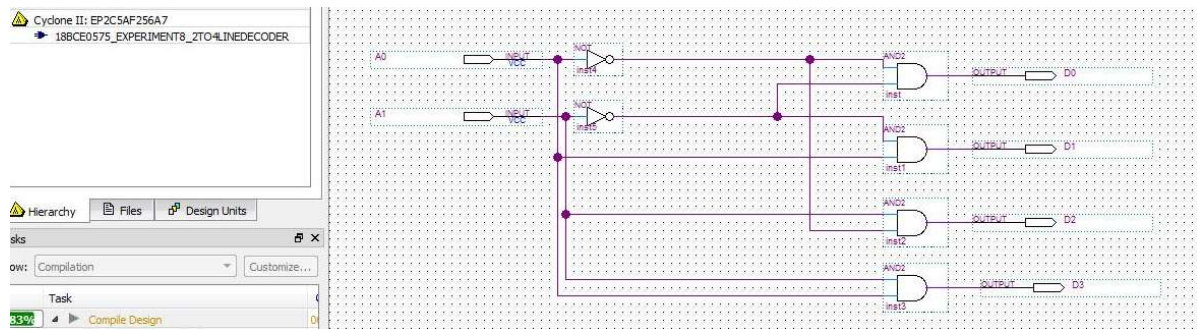


#### TRUTH TABLE:

A	B	D0	D1	D2	D3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1


#### EXPRESSIONS:

1.  $D0 = A'B'$
2.  $D1 = A'B$
3.  $D2 = AB'$
4.  $D3 = AB$

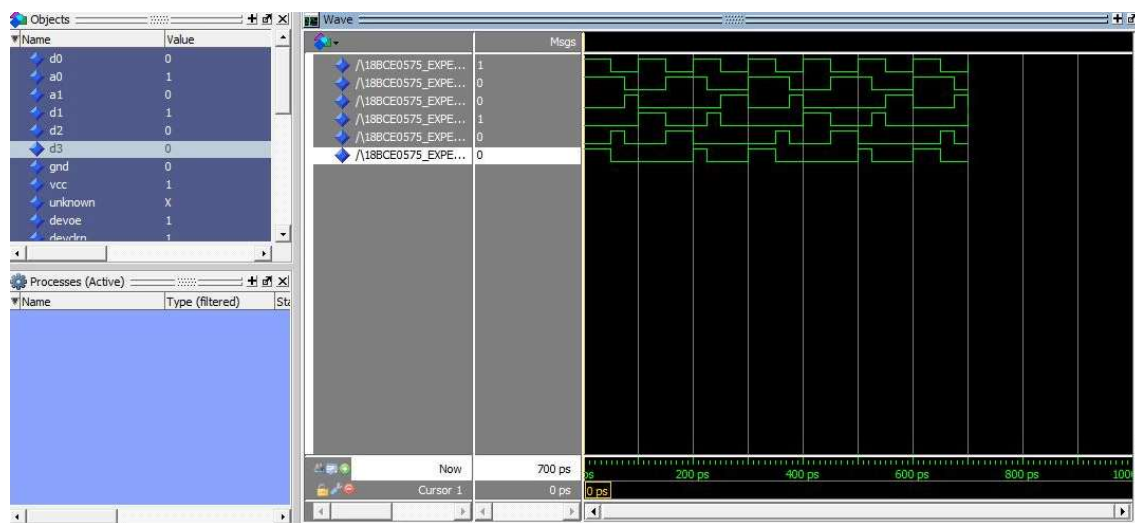**FINAL RESULT:**

- b. **AIM:** Design a logic circuit to control the traffic light as per the given details. Using the sensor outputs A,B,C and D as inputs, N-S and E-W be two outputs that go high.

### CIRCUIT DIAGRAM:

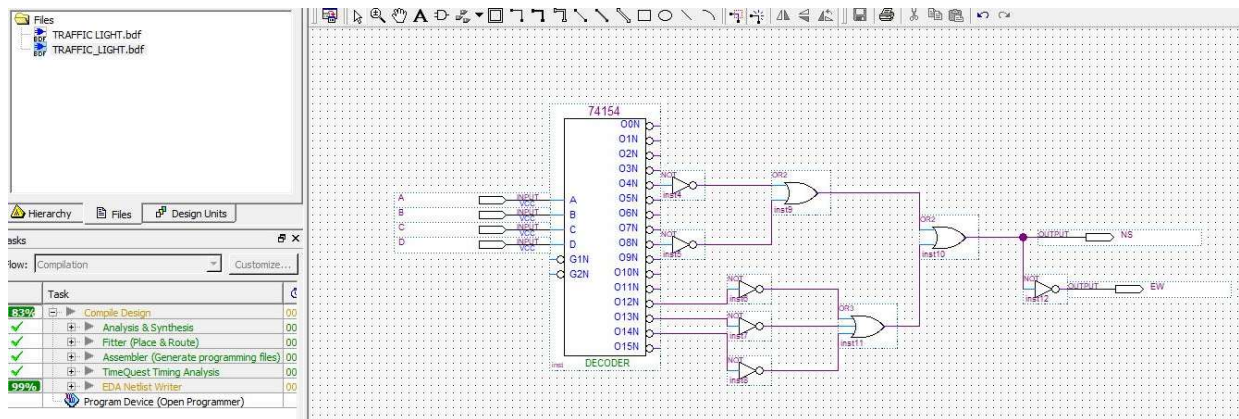

### TRUTH TABLE:


A	B	C	D	EW	NS
0	0	0	0	1	0
0	0	0	1	1	0
0	0	1	0	1	0
0	0	1	1	1	0
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	1	0
0	1	1	1	1	0
1	0	0	0	0	1
1	0	0	1	1	0
1	0	1	0	1	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	0	1	0	1
1	1	1	0	0	1
1	1	1	1	1	0



**EXPRESSIONS:**


$$NS = A'BC'D' + AB'C'D' + ABC'D' + ABCD'$$

$$ES = NS'$$

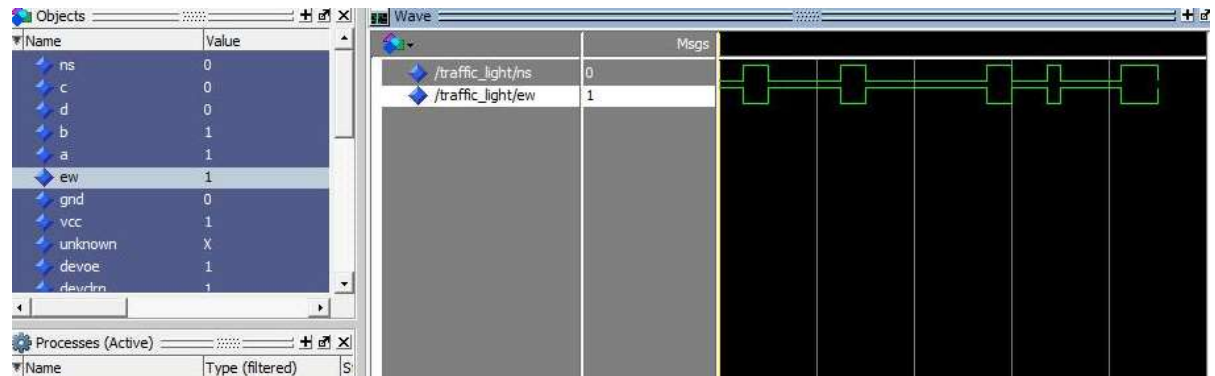**FINAL RESULT:**

c. **AIM:** Design a decimal to BCD encoder.

### CIRCUIT DIAGRAM:

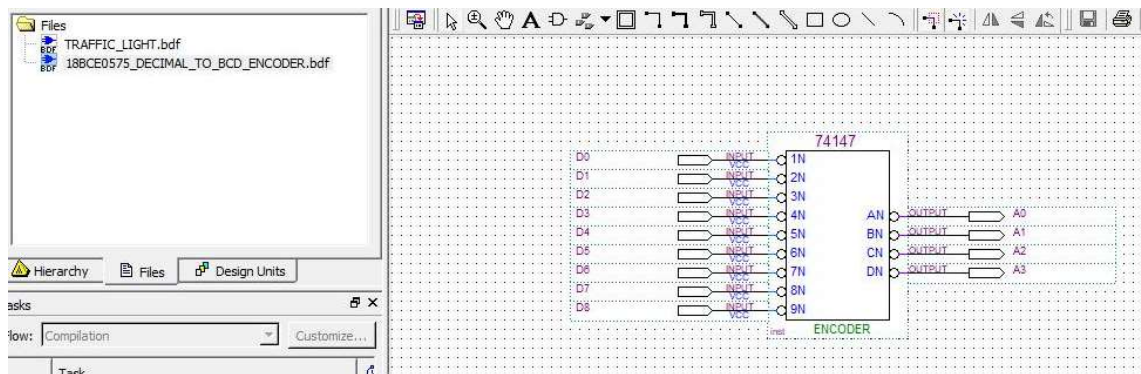

### TRUTH TABLE:

DECIMAL	A3	A2	A1	A0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1


### EXPRESSIONS:

$$A3 = D8 + D9$$

$$A2 = D4 + D5 + D6 + D7$$


$$A1 = D2 + D3 + D6 + D7$$

$$A0 = A1 + A3 + A5 + A7 + A9$$

 **FINAL RESULT:**

d. **AIM:** To design a 8 to 3 line priority encoder

### CIRCUIT DIAGRAM:

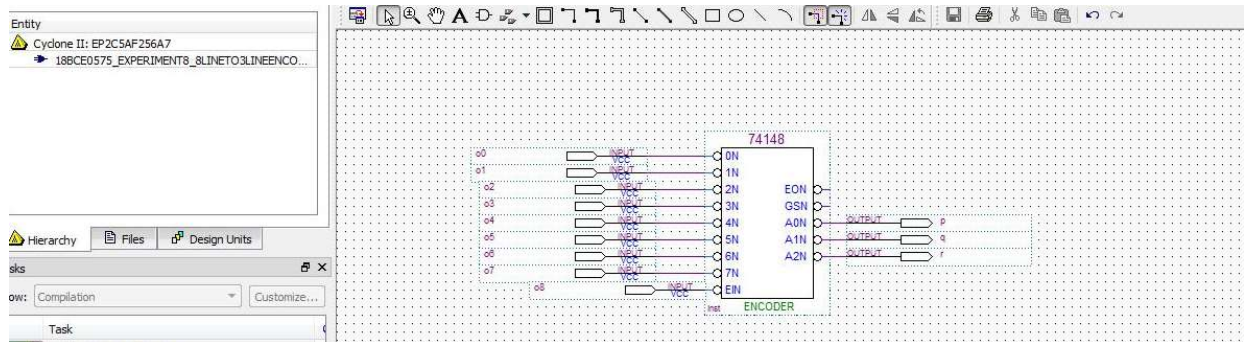

### TRUTH TABLE:


O0	O1	O2	O3	O4	O5	O6	O7	P	Q	R
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

### EXPRESSIONS:

$$P = O4 + O5 + O6 + O7$$

$$Q = O2 + O3 + O6 + O7$$

$$R = O1 + O3 + O5 + O7$$

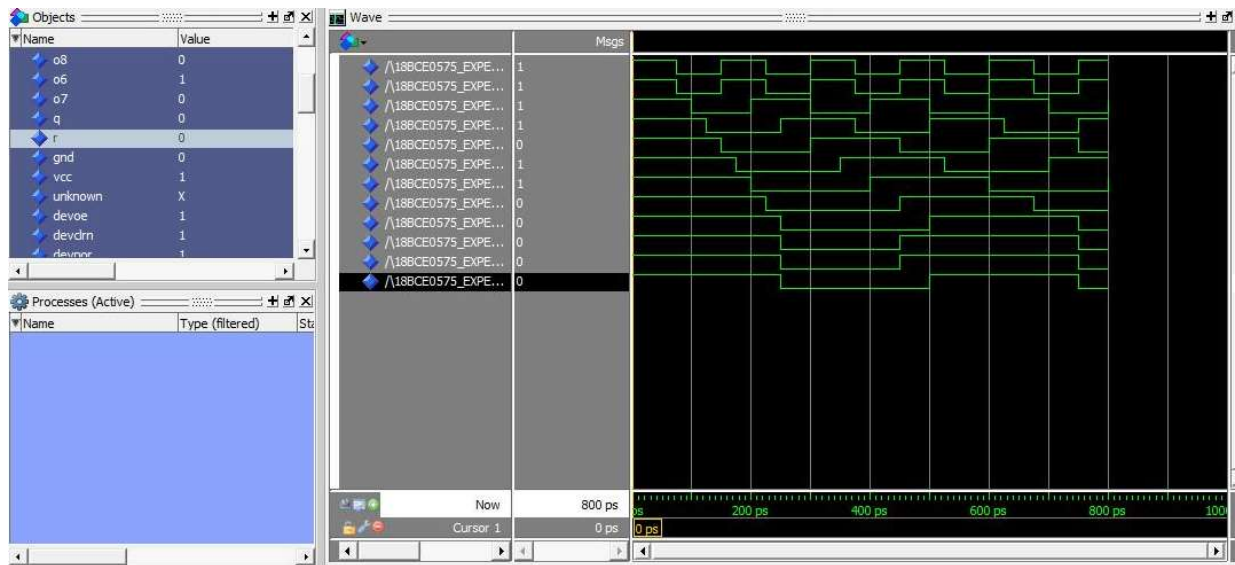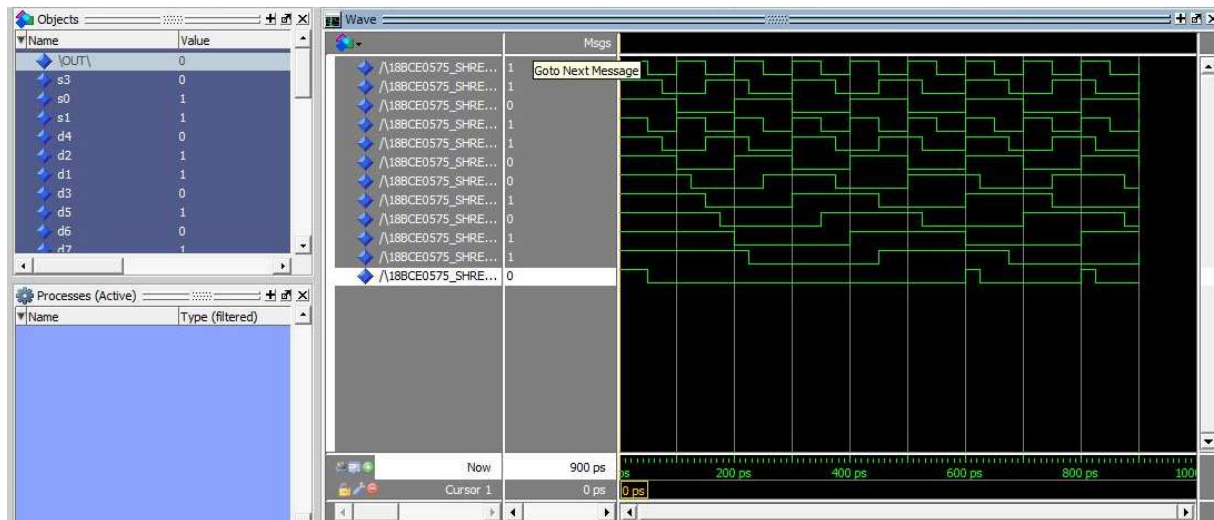
**FINAL RESULT:**

**QUESTION 4**

- a. **AIM:** 8 to 1 mux using two 4 to 1 mux and one 2 to 1 mux.


**TRUTH TABLE:**

S2	S1	S0	OUT
0	0	0	D0
0	0	1	D1
0	1	0	D2
0	1	1	D3
1	0	0	D4
1	0	1	D5
1	1	0	D6
1	1	1	D7

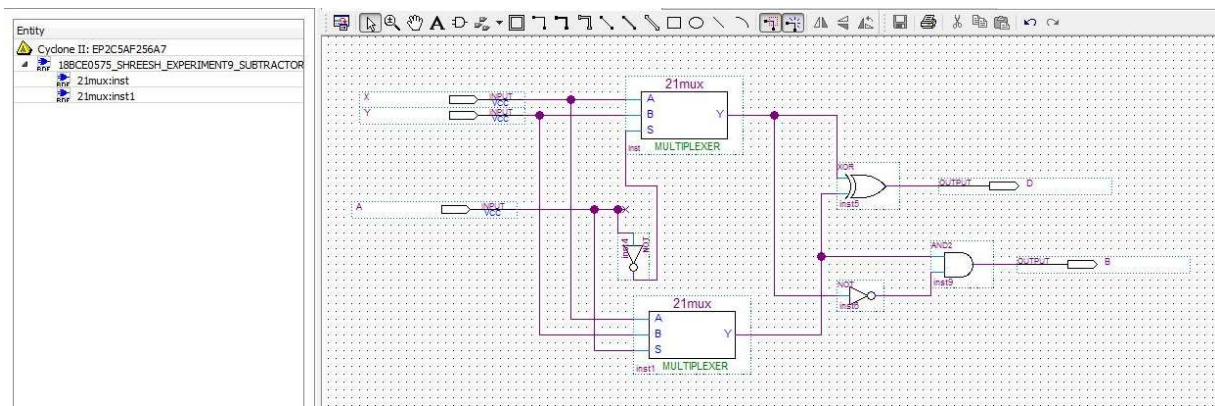**FINAL RESULT:**




**AIM:** Design a circuit which perform  $X-Y$  if  $A=1$  and  $Y-X$  if  $A=0$ .




**TRUTH TABLE:**

A	X	Y	B	D
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	0	0
1	0	0	0	0
1	0	1	1	1
1	1	0	0	1
1	1	1	0	0

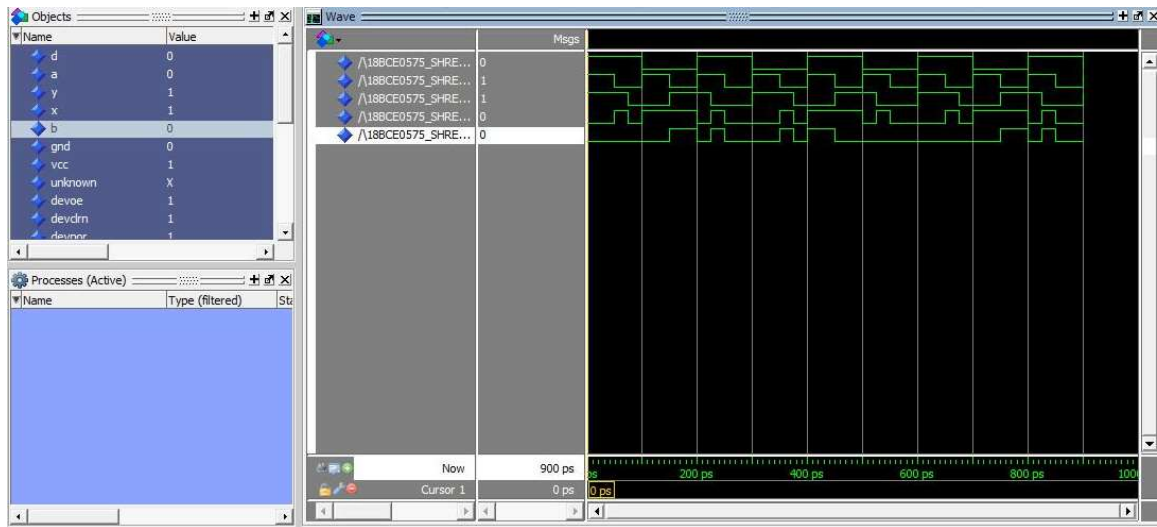 
**FINAL RESULT:**

**AIM:** Design 2 to 4 line demux using NOR gates.




**TRUTH TABLE:**

A	B	W	X	Y	Z
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

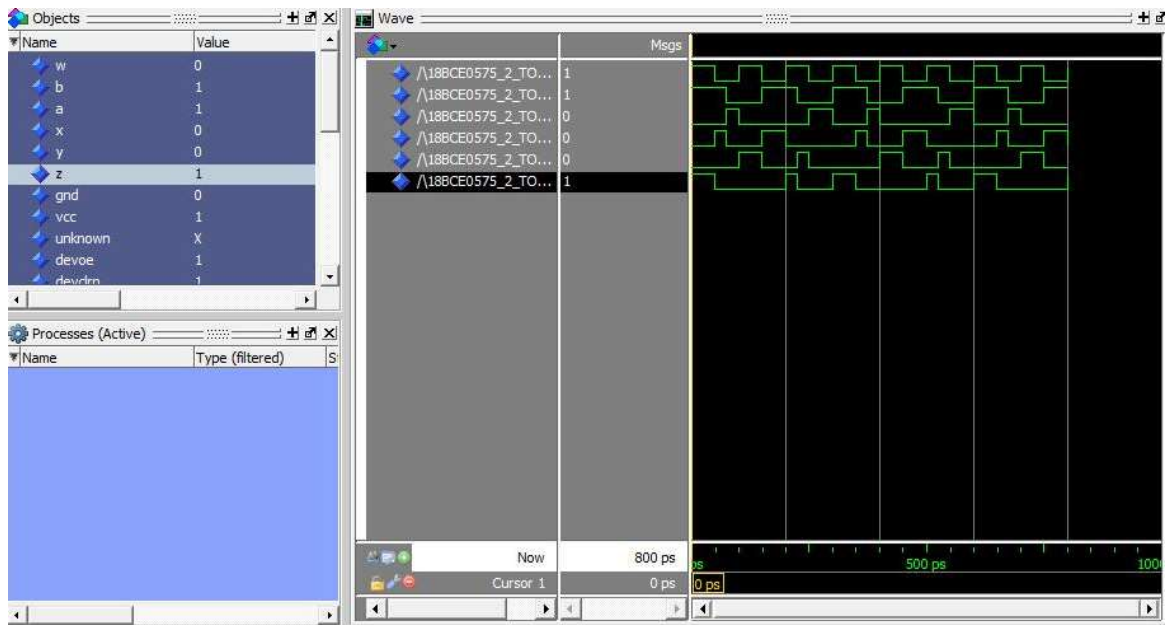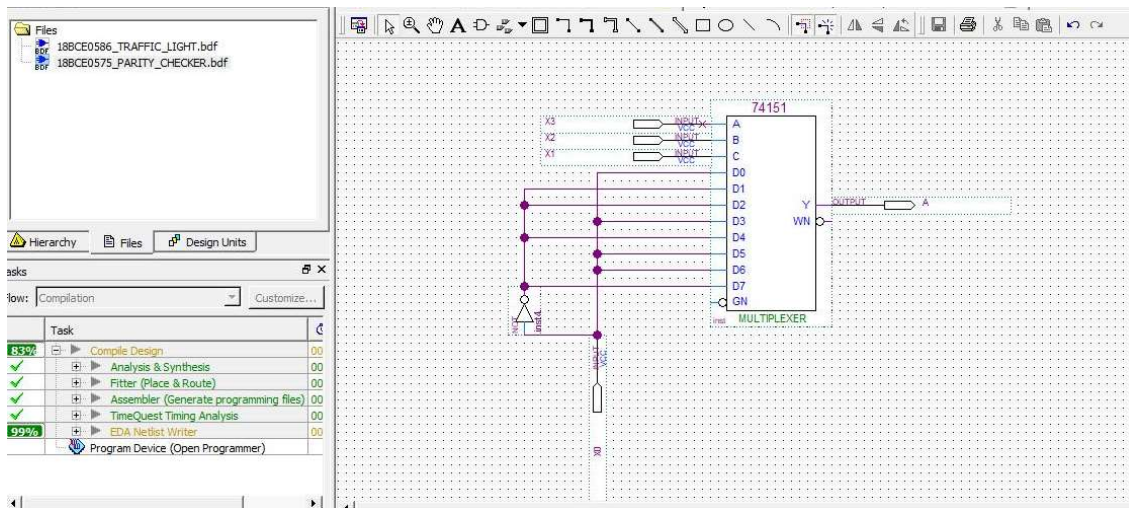**FINAL RESULT:**

**AIM:** Design a 4 bit even parity checker



**TRUTH TABLE:**

X3	X2	X1	X0	A	
0	0	0	0	0	X0
0	0	0	1	1	X0
0	0	1	0	1	X0'
0	0	1	1	0	X0'
0	1	0	0	1	X0'
0	1	0	1	0	X0'
0	1	1	0	0	X0
0	1	1	1	1	X0
1	0	0	0	1	X0'
1	0	0	1	0	X0'
1	0	1	0	0	X0
1	0	1	1	1	X0
1	1	0	0	0	X0
1	1	0	1	1	X0
1	1	1	0	1	X0'
1	1	1	1	0	X0'

**FINAL RESULT:**